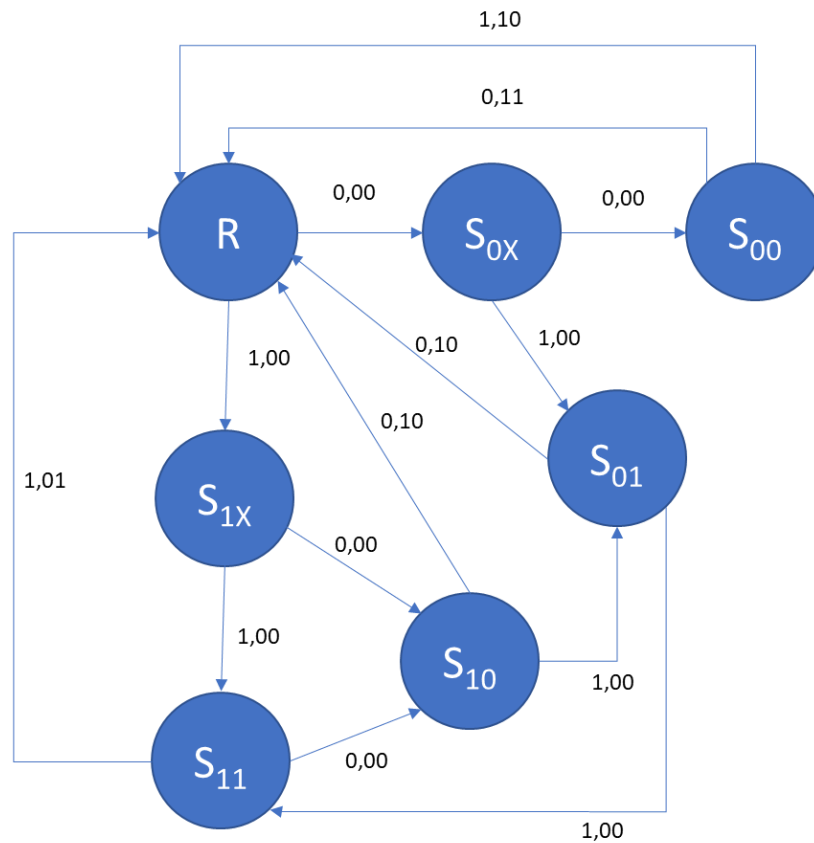


Exam - Computer Architecture Unit I [18/01/2023] (A) - Solution

Exercise 1 (8 points) Design a sequential circuit with an input x and two outputs $z1$ and $z0$. The output $z1$ must be equal to 1 if the last three bits on input contain at least two 0, whereas $z0$ must be equal to 1 if the last three bits are the same (i.e., 3 zeros or 3 ones). Do not consider overlaps. Draw the sequential circuit (use a ROM for the combinational part).

Example x 10100000111
 $z1$ 00010010000
 $z0$ 00000010001




States encoding:

R	000
S0X	001
S1X	010
S00	011
S01	100
S10	101
S11	110

Outputs and next state table:


CS	S ₂	S ₁	S ₀	x	NS	S ₂ '	S ₁ '	S ₀ '	z1	z0
R	0	0	0	0	S0X	0	0	1	0	0
R	0	0	0	1	S1X	0	1	0	0	0
S0X	0	0	1	0	S00	0	1	1	0	0
S0X	0	0	1	1	S01	1	0	0	0	0
S1X	0	1	0	0	S10	1	0	1	0	0
S1X	0	1	0	1	S11	1	1	0	0	0
S00	0	1	1	0	R	0	0	0	1	1
S00	0	1	1	1	R	0	0	0	1	0
S01	1	0	0	0	R	0	0	0	1	0
S01	1	0	0	1	S11	1	1	0	0	0
S10	1	0	1	0	R	0	0	0	1	0
S10	1	0	1	1	S01	1	0	0	0	0
S11	1	1	0	0	S10	1	0	1	0	0
S11	1	1	0	1	R	0	0	0	0	1

Circuit:

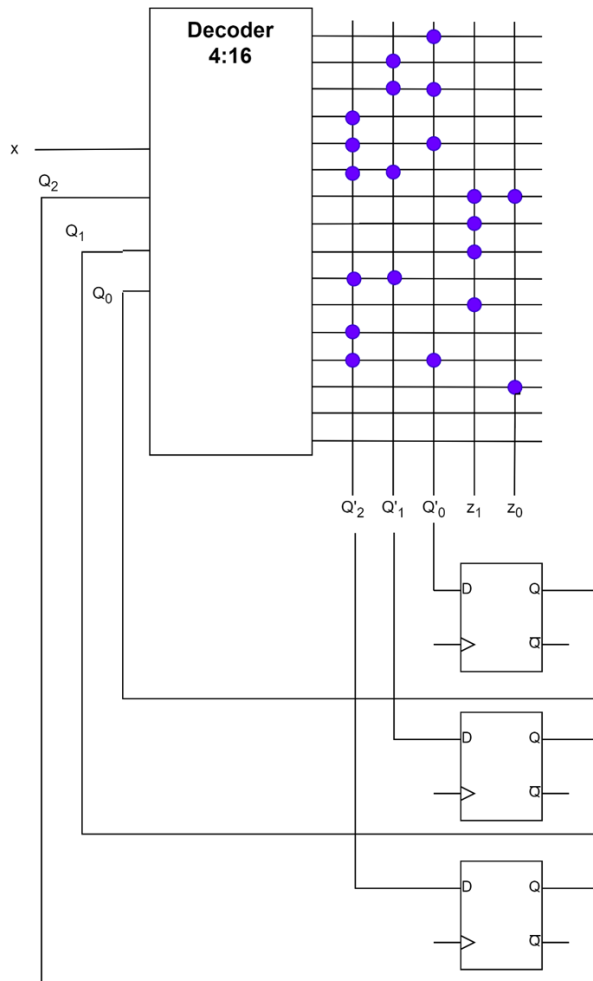

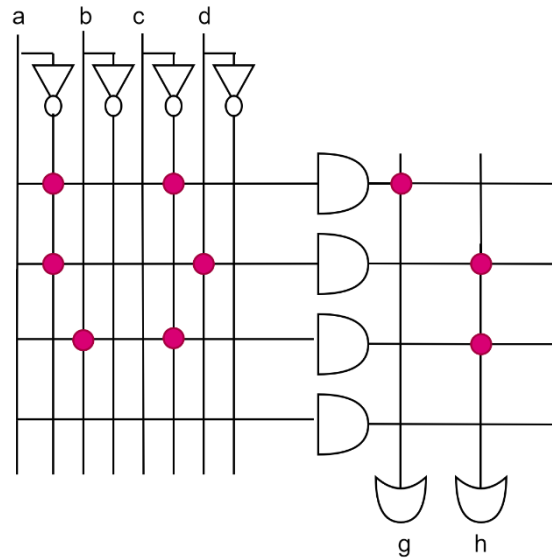Exercise 2 (1+2+1+2 points) Consider the PLA shown below.

- Write the boolean expressions for functions g and h
- Transform the boolean expression $f = g \oplus h$, using boolean algebra's axiom, rules, and theorems, in canonical SOP form
- Write down the truth table for f
- Write down the minimal SOP and POS expressions for f



$$g = \bar{a}\bar{c}$$

$$h = \bar{a}d + b\bar{c}$$

Canonical SOP form:

$$f = \bar{a}\bar{c} \oplus (\bar{a}d + b\bar{c}) = \bar{a}b\bar{c} + \bar{a}cd + \bar{a}\bar{b}\bar{c}\bar{d} = \bar{a}b\bar{c}d + \bar{a}b\bar{c}\bar{d} + \bar{a}bcd + \bar{a}\bar{b}cd + \bar{a}\bar{b}\bar{c}\bar{d}$$

Truth table for f:

a	b	c	d	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Minimal SOP:

a b		00	01	11	10
c d	00	1	0	1	0
	01	0	0	1	0
	11	1	1	0	0
	10	0	0	0	0


$$f = \bar{a}\bar{b}\bar{c}\bar{d} + ab\bar{c} + \bar{a}cd$$

Minimal POS:

a b		00	01	11	10
c d	00	1	0	1	0
	01	0	0	1	0
	11	1	1	0	0
	10	0	0	0	0

$$f = (\bar{a} + b)(\bar{c} + d)(\bar{a} + \bar{c})(a + c + \bar{d})(a + \bar{b} + c)$$

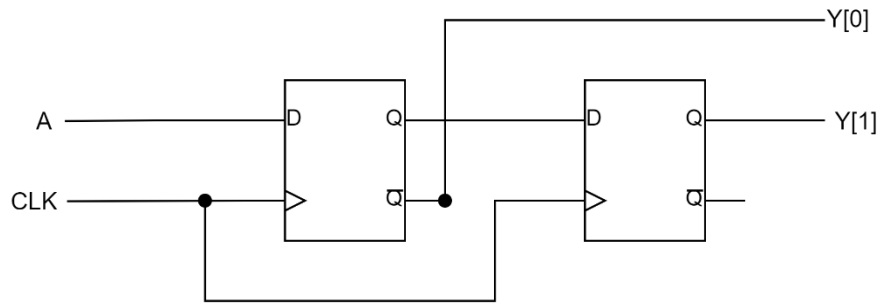Exercise 3 (4 points) Describe the following circuit using SystemVerilog:



```
module esercizio5(input logic clk,
                  input logic A,
                  output logic[1:0] Y);
```

```
    logic net;
    always_ff @(posedge clk)
    begin
        Y[0] <= ~A;
        net <= A;
        Y[1] <= net;
    end
```

```
endmodule
```


Exercise 4 (3 points)

A circuit receives the boolean inputs a, b, c, d and produces an output y such that:

$$y=1 \quad \text{if} \quad a \cdot b = 1 \text{ or } \bar{b} + \bar{c} = 0 \text{ or } \bar{a}\bar{b}\bar{c} = 1$$

- Write down the truth table
- Implement y with a 4-to-1 MUX using inputs a e b as control variables
- Draw the circuit corresponding to the NAND-NAND equation for the given circuit

a	b	c	d	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

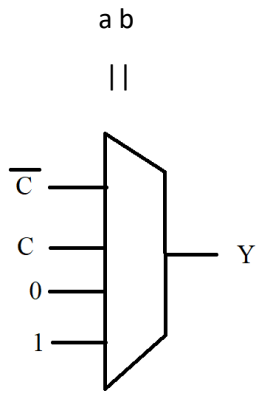


NAND-NAND:

Minimal POS: $A'B'C' + BC + AB$

NAND-NAND = $((A'B'C')' (BC)' (AB)')'$

Circuit:

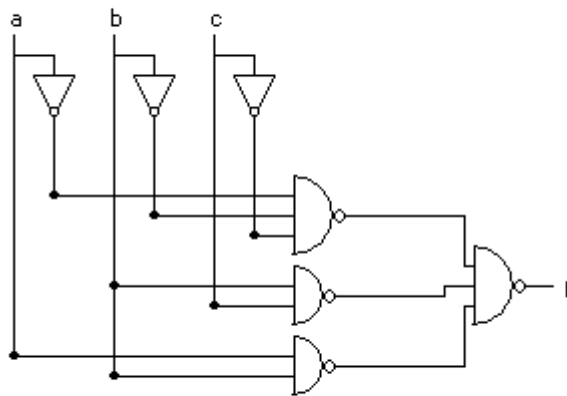

Exercise 5 (1+2+1 points)

Represent $A = -3.25$ using the IEEE half-precision floating point standard. Sum A and B (using the algorithm for summing IEEE floating point numbers), with $B = 0100_0110_0100_0000$ and represent the result as a IEEE half-precision floating point number. Last, represent the 16-bits of the result in hexadecimal format.

$$A = -3.25 \rightarrow -11.01_2 = -1 \cdot 2^1 \cdot 1.101_2$$

Sign = 1 (negative)

Exponent = 1

Exponent+bias = $1+15 = 16 = 10000_2$

Mantissa = 1010000000

$A = 1100_0010_1000_0000$

B:

Sign = 0 (positive)

Exponent+bias = $10001_2 = 17$

Exponent = $17-15 = 2$

Mantissa = 1001000000₂

$$B = 1 \cdot 2^2 \cdot 1.1001_2 = 110.01_2 \rightarrow 6.25$$

A+B – Shift and sum mantissas

$$11.0011 + (x 2^2)$$

$$01.1001 = (x 2^2)$$

$$00.1100 \quad (x 2^2)$$

$$= 11.00_2 = 3_{10} = 1.100_2 \times 2^1$$

Sign = 0 (positive)

Exponent = 1

$$\text{Exponent} + \text{bias} = 1 + 15 = 16 = 10000_2$$

Mantissa = 1000000000

IEEE Representation = 0100_0010_0000_0000 = 0x4200

Exercise 6 (5 points) Given the function $f = \bar{a}d \oplus (a\bar{b} + bc)$

Represent it in POS form using Boolean algebra axiom, rules, and theorems.

$$\begin{aligned} f &= (d\bar{a}) \oplus (a\bar{b} + bc) = \\ d\bar{a}(\overline{a\bar{b} + bc}) + \overline{d\bar{a}}(a\bar{b} + bc) &= d\bar{a} \cdot (\overline{a\bar{b}}) \cdot (\overline{bc}) + (\bar{d} + a)(a\bar{b} + bc) = \\ d \cdot \bar{a} \cdot (\bar{a} + b) \cdot (\bar{b} + \bar{c}) + (\bar{d} + a)(a\bar{b} + bc) &= \\ d \cdot \bar{a} \cdot (\bar{b} + \bar{c}) + (\bar{d} + a)(a + b)(a + c)(\bar{b} + c) &= \\ = (a + b + d)(a + c + d)(\bar{b} + c + d)(\bar{a} + \bar{b} + c)(a + \bar{b} + \bar{c} + \bar{d}) \end{aligned}$$