



# 5 - Logic Circuits

Tuesday, May 14, 2024

9:15 PM

## LOGIC CIRCUITS

\* is composed of

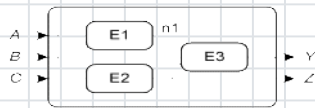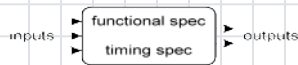

• Nodes - inputs - A, B, C internal - n1  
Outputs - Y, Z

• Elements - E1, E2, E3

## ★ TYPES OF LOGIC

⇒ Sequential Logic - has memory


- Outputs are determined by previous and current values of inputs

⇒ Combinational Logic


- Memoryless

- Output is determined by current values of input.

• eg - gates

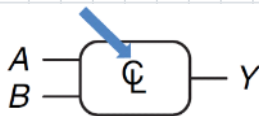


eg -

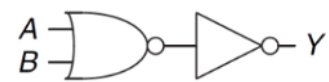
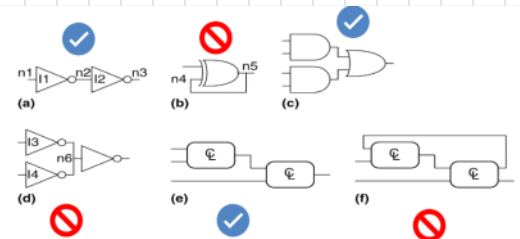
## ★ Rules to build combinational circuit

- Every element is combinational
- Every node is either an input or connects to exactly one output of an element
- The circuit contains no cyclic paths



## ⇒ Boolean Equations

Functional specification of outputs in terms of inputs

eg -  $C_{out} = F(A, B, c_{in})$  w/c could be  $C_{out} = AB + AC_{in} + Bc$

• N.B - OR = SUM

- AND = PRODUCT

- Complement = INVERSE

- Literal - a variable or its complement  $\{A, \bar{A}, B, c, \bar{c}\}$

- Implicant - and of one or more literals

$AB\bar{c}, AB, \bar{c}B$

- Min term - product that includes all input variables

$ABC, \bar{A}B\bar{c}, \bar{A}Bc$

- Max term - sum that includes all input variables

$(A + B + c), (\bar{A} + B + \bar{c}), (\bar{A} + \bar{B} + \bar{c})$

## \* Operator Precedence

NOT → AND → OR