

Exam - Computer Architecture Unit I [01/02/2024] (A)

Surname: _____ Name: _____


Student ID Number (Matricola): _____

DSA Students should solve only the first 4 exercises (grade will be scaled accordingly)


Exercise 1 (7 points) Design an FSM with an input x and an output y . The FSM outputs y when the last 3 bits, interpreted as a two's complement number, represent a negative number, or a number that is a multiple of 4. Do not consider overlaps. If the FSM didn't receive yet 3 bits, it outputs 0. Write down the circuit using a ROM for the combinational part.

Solution:




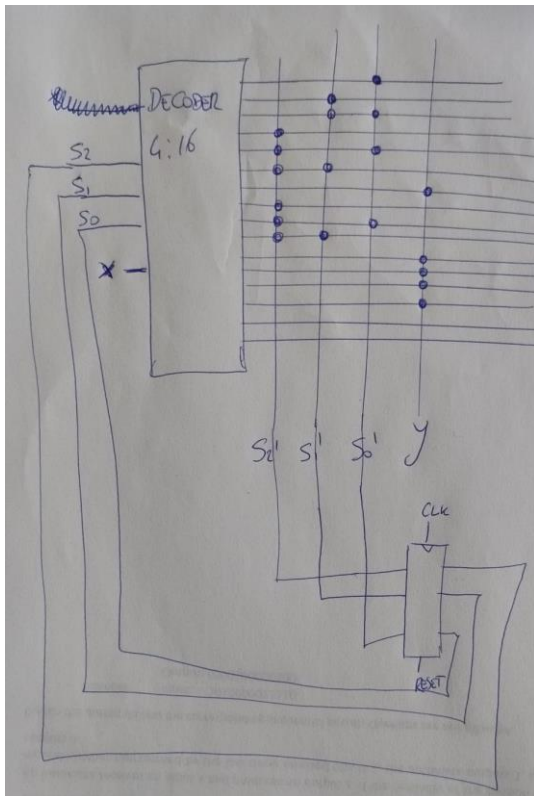

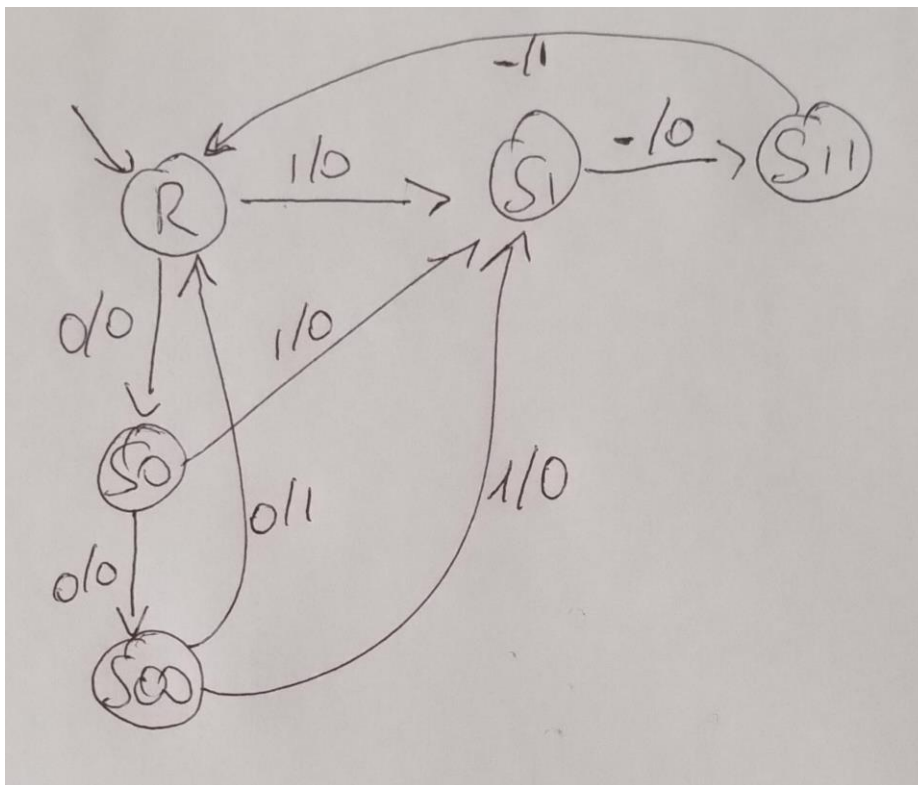Note: Can also be solved using 5 states only (diagram shown below)



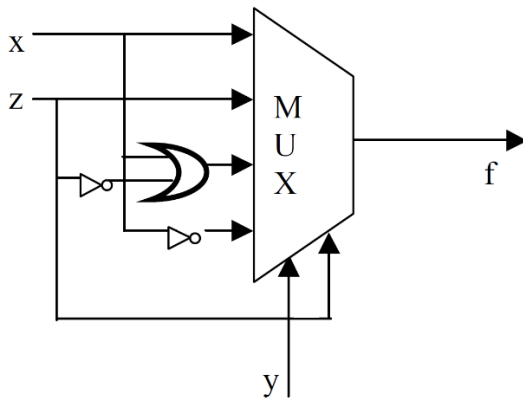Exercise 2 (6 points) Write the function f described by the following circuit; then derive the minimal SOP and POS forms using K-maps; write down the all-NAND and all-NOR forms.



$$f = (\bar{y}\bar{z})x + (\bar{y}z)z + (y\bar{z})(x+\bar{z}) + (yz)\bar{x} =$$

$$= x\bar{y}\bar{z} + \bar{y}z + xy\bar{z} + y\bar{z} + \bar{x}yz$$

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

xy \ z	00	01	11	10
0	0	1	1	1
1	1	1	0	1

$$\text{POS} = (x+y+z)(\bar{x}+\bar{y}+\bar{z})$$

$$\text{SOP} = \bar{x}\bar{z} + y\bar{z} + x\bar{y}$$

$$\text{ALL-NAND} = \overline{\bar{x}\bar{z} + y\bar{z} + x\bar{y}} = \overline{\bar{x}\bar{z}} \cdot \overline{y\bar{z}} \cdot \overline{x\bar{y}}$$

$$\text{ALL-NOR} = \overline{(x+y+z)(\bar{x}+\bar{y}+\bar{z})} = \overline{(x+y+z)} + \overline{(\bar{x}+\bar{y}+\bar{z})}$$

Exercise 3 (4 points) Encode $X = -129,125$ as an IEEE 754 half-precision number. Then compute $Z = X + Y$, where $Y = \langle 0; 00110; 1110001100 \rangle$ in IEEE 754 half-precision format. Then convert the bits of Z to a base-16 number.

Handwritten solution for Exercise 3:

$X = -129,125 = 1.0000001001 \times 2^7$

SIGN = 1
 EXPONENT = $7 + 15 = 22$
 MANTISSA = 0000001001

$Y = + 1.1110001100 \times 2^{-9} = 0.00 \dots 01110001100 \times 2^7$
 (16 bits)

We only have 10 bits for the mantissa,
 thus $Y = 0$, and $Z = X + Y = X$

$Z = X = 1 \ 10110 \ 0000001001 = 0x D809$
 (D 8 0 9)


Exercise 4 (5 points) Describe in SystemVerilog an 8-bits shift register with synchronous reset and parallel load.

Solution

```
module shiftreg(input logic clk,
               input logic reset, load,
               input logic sin,
               input logic [7:0] d,
               output logic [7:0] q,
               output logic sout);
    always_ff @(posedge clk)
        if (reset) q <= 0;
        else if (load) q <= d;
        else q <= {q[N-2:0], sin};
    assign sout = q[N-1];
endmodule
```

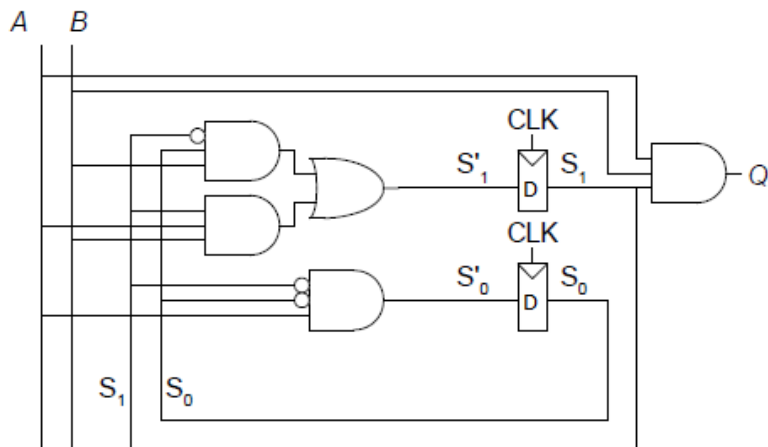
Exercise 5 (5 points)

Analyze the following sequential circuit and draw the corresponding FSM. Then write down a sequence of input bits that, for the last bit, would produce an output equal to 1.



Solution:

$$S'_1 = \overline{S_1}S_0B + S_1AB$$

$$S'_0 = \overline{S_1}\overline{S_0}A$$

$$Q' = S_1AB$$

Transition table

current state		inputs		next state		output
s_1	s_0	a	b	s'_1	s'_0	q
0	0	0	X	0	0	0
0	0	1	X	0	1	0
0	1	X	0	0	0	0
0	1	X	1	1	0	0
1	0	1	1	1	0	1
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	0	0	0

State encoding

state	encoding $s_1:s_0$
S0	00
S1	01
S2	10

State transition diagram:

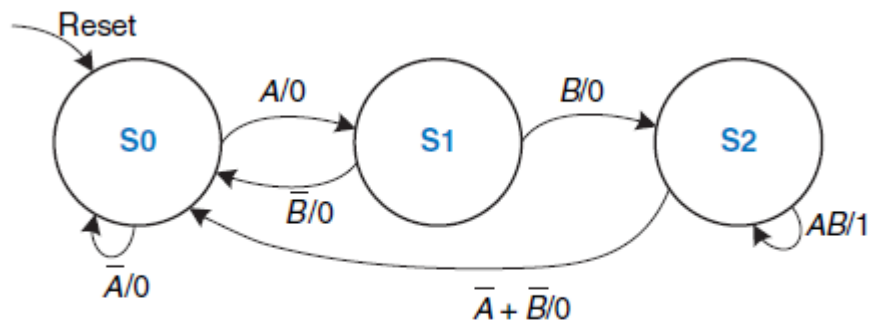


Figure 3.70 State transition diagram

Exercise 6 (3 points)

Using Boolean's algebra theorems and axioms, simplify the following equation:

$$(a\bar{b} + \overline{bc} + c(\bar{a} + b)) \oplus ac$$

Solution:

(You could also solve it in fewer steps by simplifying first $(B'C + C(A'+B))' = (B'C + A'C + BC)' = (C + A'C)' = C'$)

Handwritten solution for Exercise 6:

$$\begin{aligned} & (\overline{a\bar{b} + \overline{bc} + c(\bar{a} + b)}) \oplus ac = \\ & = (\overline{a\bar{b} + \overline{bc} \cdot c(\bar{a} + b)}) \oplus ac = \\ & = (\overline{a\bar{b} + (b + \bar{c}) \cdot (\bar{c} + \overline{\bar{a} + b})}) \oplus ac = \\ & = (\overline{a\bar{b} + (b + \bar{c})(\bar{c} + a\bar{b})}) \oplus ac = \\ & = (\overline{a\bar{b} + \cancel{b\bar{c}} + \bar{c} + \cancel{a\bar{b}\bar{c}}}) \oplus ac = \\ & = (\overline{a\bar{b} + \bar{c}}) \oplus ac = \\ & = \overline{(\overline{a\bar{b} + \bar{c}})ac} + (\overline{a\bar{b} + \bar{c}})\overline{ac} = \\ & = \overline{(\overline{a\bar{b}} \cdot \bar{c})ac} + (\overline{a\bar{b} + \bar{c}})(\bar{a} + \bar{c}) = \\ & \quad \cancel{\overline{(\bar{a} + b)ac}} \\ & = (\bar{a} + b)ac + \cancel{a\bar{b}\bar{c}} + \cancel{\bar{a}\bar{c}} + \bar{c} = \\ & = abc + \bar{c} = \\ & = ab + \bar{c} \end{aligned}$$