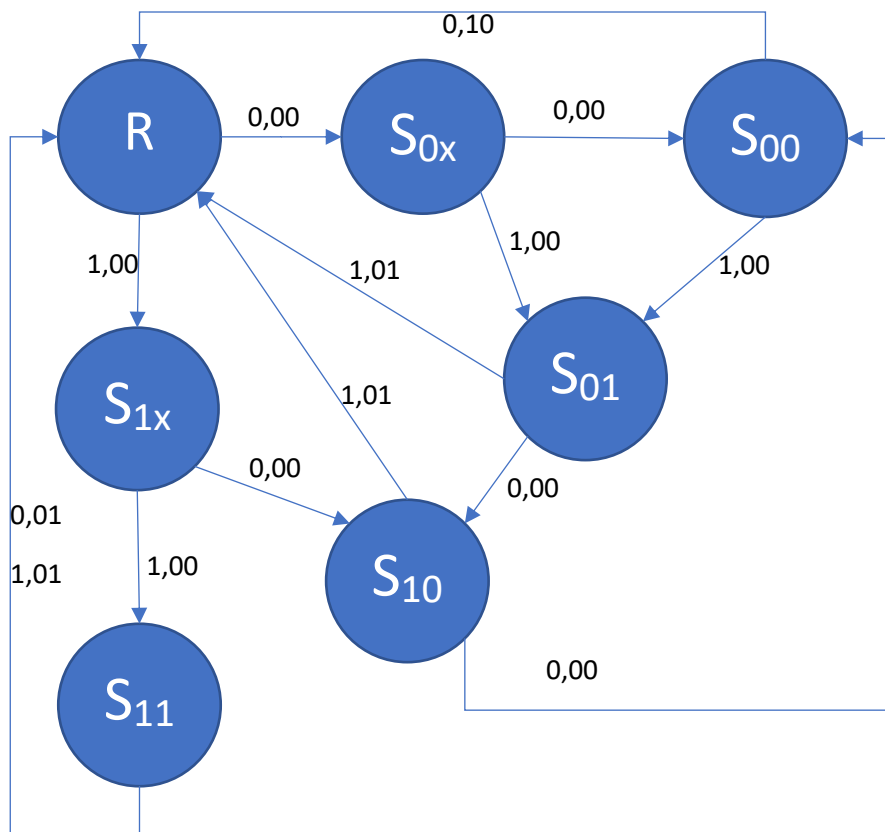


Exam - Computer Architecture Unit I [18/01/2023] (B) - Solution

Esercizio 1 (8 punti) Design a sequential circuit with an input x and two outputs $z1$ and $z0$. The output $z1$ must be equal to 1 if the last three bits on input are all equal to 0, whereas $z0$ must be equal to 1 if the last three bits contain at least two 1s. Do not consider overlaps. Draw the sequential circuit (use a ROM for the combinational part).

Example x 000001011100
 $z1$ 001000000000
 $z0$ 0000000010010



States encoding:

R	000
S0X	001
S1X	010
S00	011
S01	100
S10	101
S11	110

Outputs and next state table:


CS	S ₂	S ₁	S ₀	x	NS	S ₂ '	S ₁ '	S ₀ '	z1	z0
R	0	0	0	0	S0X	0	0	1	0	0
R	0	0	0	1	S1X	0	1	0	0	0
S0X	0	0	1	0	S00	0	1	1	0	0
S0X	0	0	1	1	S01	1	0	0	0	0
S1X	0	1	0	0	S10	1	0	1	0	0
S1X	0	1	0	1	S11	1	1	0	0	0
S00	0	1	1	0	R	0	0	0	1	0
S00	0	1	1	1	S01	1	0	0	0	0
S01	1	0	0	0	S10	1	0	1	0	0
S01	1	0	0	1	R	0	0	0	0	1
S10	1	0	1	0	S00	0	1	1	0	0
S10	1	0	1	1	R	0	0	0	0	1
S11	1	1	0	0	R	0	0	0	0	1
S11	1	1	0	1	R	0	0	0	0	1

Circuit:

Same as track A, but with different dots on the ROM.

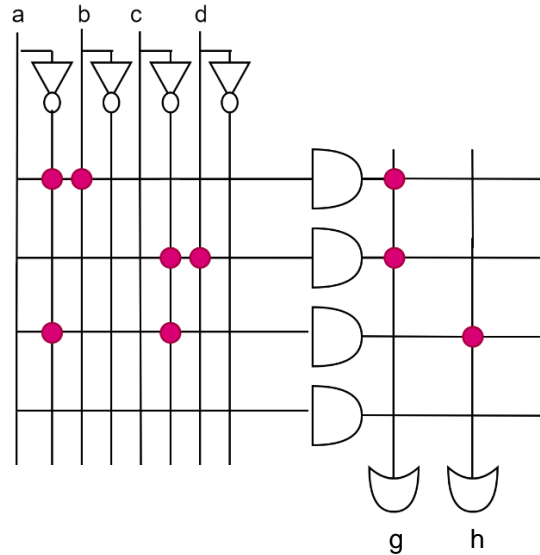Exercise 2 (1+2+1+2 points) Consider the PLA shown below.

- Write the boolean expressions for functions g and h
- Transform the boolean expression $f = g \oplus h$, using boolean algebra's axiom, rules, and theorems, in canonical SOP form
- Write down the truth table for f
- Write down the minimal SOP and POS expressions for f



$$h = \bar{a}\bar{c}$$

$$g = \bar{a}b + \bar{c}d$$

Canonical SOP form

$$\begin{aligned}
 f &= \bar{a}\bar{c} \oplus (\bar{a}b + \bar{c}d) = \overline{(\bar{a}\bar{c})}(\bar{a}b + \bar{c}d) + (\bar{a}\bar{c})\overline{(\bar{a}b + \bar{c}d)} \\
 &= (a + c)(\bar{a}b + \bar{c}d) + (\bar{a}\bar{c})((\bar{a}b) \cdot (\bar{c}d)) = \bar{a}bc + a\bar{c}d + (\bar{a}\bar{c})((a + b)(c + d)) \\
 &= \bar{a}bc + a\bar{c}d + (\bar{a}\bar{c})(ac + \bar{b}c + a\bar{d} + \bar{b}\bar{d}) = a\bar{c}d + \bar{a}bc + \bar{a}\bar{b}\bar{c}\bar{d} \\
 &= ab\bar{c}d + a\bar{b}\bar{c}d + \bar{a}b\bar{c}d + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}\bar{c}d
 \end{aligned}$$

Truth table for f:

a	b	c	d	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Minimal SOP:

a b		00	01	11	10
c d	00	1	0	0	0
	01	0	0	1	1
	11	0	1	0	0
	10	0	1	0	0


$f = \bar{a}\bar{b}\bar{c}\bar{d} + a\bar{c}d + \bar{a}bc$

Minimal POS:

a b		00	01	11	10
c d	00	1	0	0	0
	01	0	0	1	1
	11	0	1	0	0
	10	0	1	0	0

$$f = (\bar{a} + d)(b + \bar{c})(\bar{a} + \bar{c})(a + \bar{b} + c)(a + c + \bar{d})$$

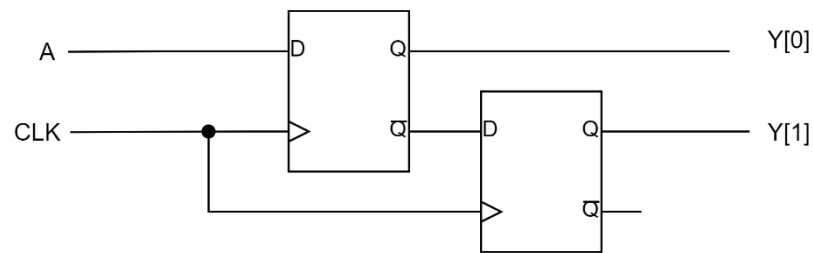Exercise 3 (4 points) Describe the following circuit using SystemVerilog:



```
module esercizio5(input logic clk,
                  input logic A,
                  output logic[1:0] Y);
```

```
  logic net;
```

```
    always_ff @(posedge clk)
```

```
    begin
```

```
        Y[0] <= A;
```

```
        Y[1] <= ~Y[0];
```

```
    end
```

```
endmodule
```


Exercise 4 (3 points)

A circuit receives the boolean inputs a, b, c, d and produces an output y such that:

$$y=1 \quad \text{if} \quad a \cdot \bar{b} = 1 \text{ or } b + \bar{d} = 0 \text{ or } \bar{a}b\bar{d} = 1$$

- Write down the truth table
- Implement y with a 4-to-1 MUX using inputs a e b as control variables
- Draw the circuit corresponding to the NAND-NAND equation for the given circuit


a	b	c	d	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

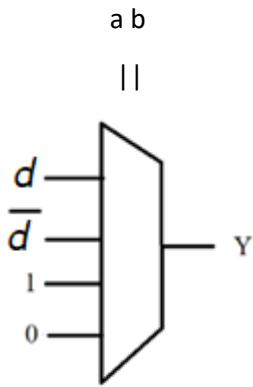

NAND-NAND

Minimal POS: $B'D + A'BD' + AB'$

NAND-NAND: $((B'D)'(A'BD')'(AB')')'$

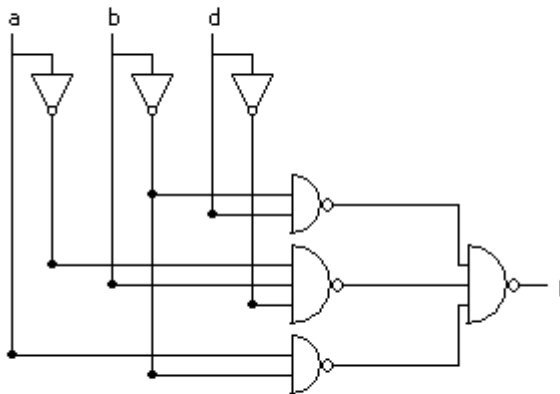

Exercise 5 (1+2+1 points)

Represent $A = 3.75$ using the IEEE half-precision floating point standard. Sum A and B (using the algorithm for summing IEEE floating point numbers), with $B = 1100_0110_1100_0000$ and represent the result as a IEEE half-precision floating point number. Last, represent the 16-bits of the result in hexadecimal format.

$$A = 3.75 \rightarrow 11.11_2 = 1 \cdot 2^1 \cdot 1.111_2$$

Sign = 0 (positive)

Exponent = 1

Exponent+bias = $1+15 = 16 = 10000_2$

Mantissa = 1110000000

$A = 0100_0011_1000_0000$

B:

Sign = 1 (negative)

Exponent+bias = $10001_2 = 17$

Exponent = $17-15 = 2$

Mantissa = 1011000000₂

$$B = -1 \cdot 2^2 \cdot 1.1011_2 = 110.11_2 \rightarrow -6.75$$

A+B – Shift and sum mantissas

$$00.1111 + (x 2^2)$$

$$10.0101 = (x 2^2)$$

$$11.0100 \quad (x 2^2)$$

$$= -00.11_2 \times 2^2 = -11.0_2 = -3_{10} = -1.100_2 \times 2^1$$

Sign = 1 (negative)

Exponent = 1

$$\text{Exponent} + \text{bias} = 1 + 15 = 16 = 10000_2$$

$$\text{Mantissa} = 1000000000$$

$$\text{IEEE representation} = 1100_0010_0000_0000 = 0xC200$$

Exercise 6 (5 points) Given the function

$$f = \bar{b}c \oplus (\bar{a}b + ad)$$

Represent it in POS form using Boolean algebra axiom, rules, and theorems.

$$f = (\bar{b}c) \oplus (\bar{a}b + ad) =$$

$$\bar{b}c(\overline{\bar{a}b + ad}) + \overline{\bar{b}c}(\bar{a}b + ad) = \bar{b}c \cdot (\overline{\bar{a}b}) \cdot (\overline{ad}) + (b + \bar{c})(\bar{a}b + ad) =$$

$$c \cdot \bar{b} \cdot (a + \bar{b}) \cdot (\bar{a} + \bar{d}) + (b + \bar{c})(\bar{a}b + ad) =$$

$$c \cdot \bar{b} \cdot (\bar{a} + \bar{d}) + (b + \bar{c})(\bar{a} + d)(a + b)(b + d) =$$

$$= (\bar{a} + c + d)(a + b + c)(b + c + d)(\bar{a} + \bar{b} + d)(\bar{a} + b + \bar{c} + \bar{d})$$